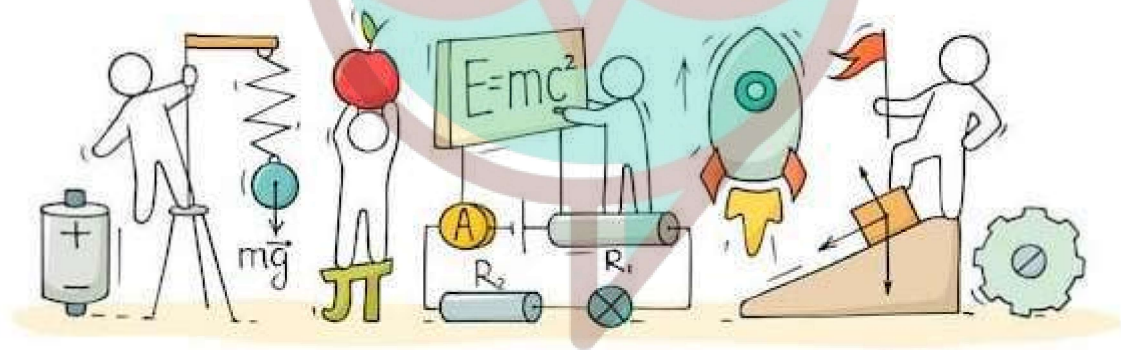


# PHYSICS



*Swotters*


## Important Questions

### Multiple Choice questions-

1. Alternating voltage ( $V$ ) is represented by the equation



- (a)  $V(t) = V_m e^{\omega t}$   
 (b)  $V(t) = V_m \sin \omega t$   
 (c)  $V(t) = V_m \cot \omega t$   
 (d)  $V(t) = V_m \tan \omega t$


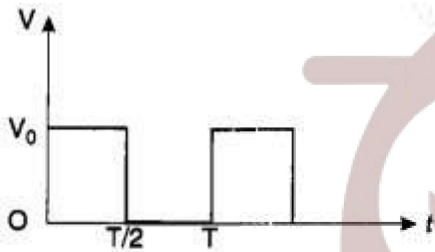
2. The rms value of potential difference  $V$  shown in the figure is



- (a)  $\frac{V_0}{\sqrt{3}}$     (b)  $V_0$     (c)  $\frac{V_0}{\sqrt{2}}$     (d)  $\frac{V_0}{2}$

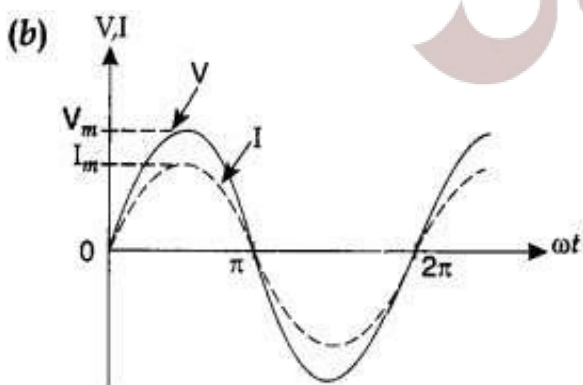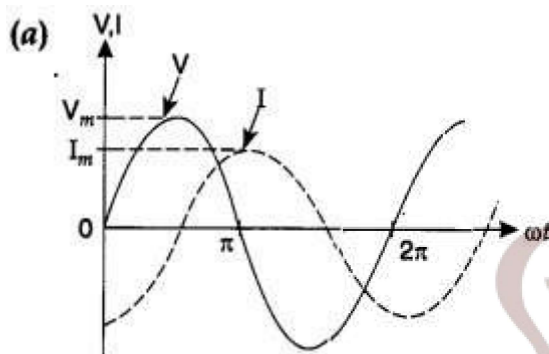3. The phase relationship between current and voltage in a pure resistive circuit is best represented by







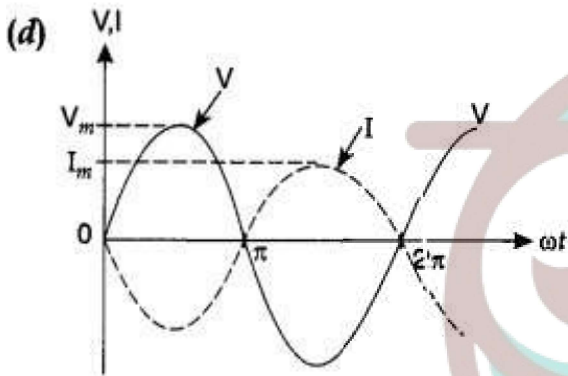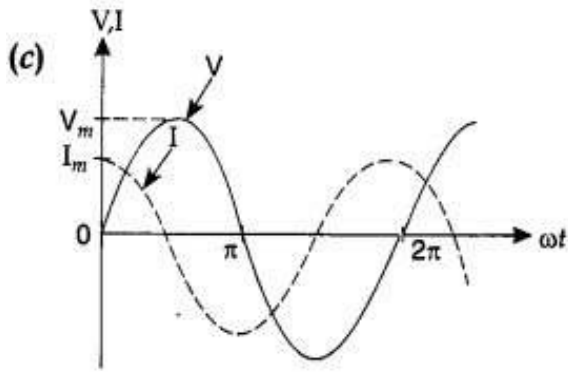

4. In the case of an inductor

- (a) voltage lags the current by  $\frac{\pi}{2}$   
 (b) voltage leads the current by  $\frac{\pi}{2}$   
 (c) voltage leads the current by  $\frac{\pi}{3}$   
 (d) voltage leads the current by  $\frac{\pi}{4}$

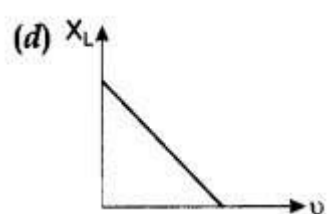
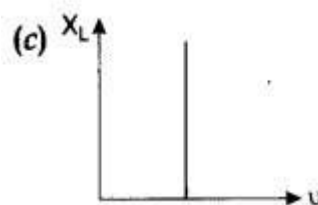
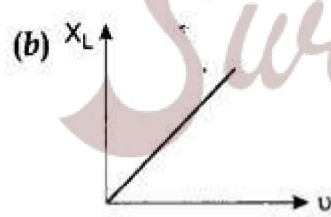
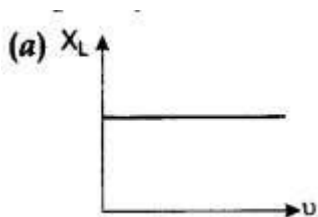
5. Which of the following graphs represents the correct variation of inductive reactance  $X_L$  with frequency  $\nu$ ?



6. In a pure capacitive circuit if the frequency of ac source is doubled, then its capacitive reactance will be

- (a) remains same
- (b) doubled
- (c) halved
- (d) zero

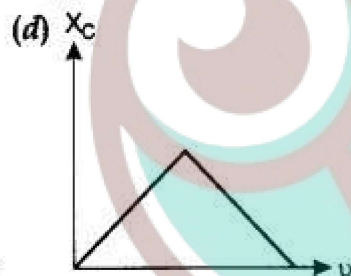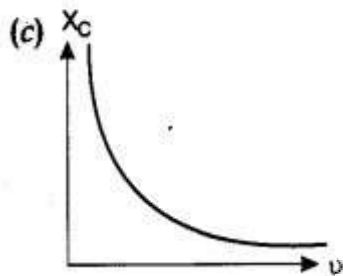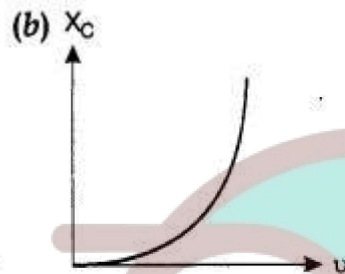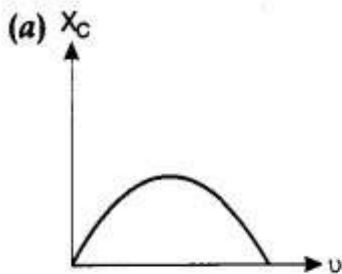7. Which of the following graphs represents the correct variation of capacitive reactance  $X_c$  with frequency  $\nu$  u?



8. In an alternating current circuit consisting of elements in series, the current increases on increasing the frequency of supply. Which of the following elements are likely to constitute the circuit?

- (a) Only resistor
- (b) Resistor and inductor
- (c) Resistor and capacitor
- (d) Only inductor

9. In which of the following circuits the maximum power dissipation is observed?

- (a) Pure capacitive circuit
- (b) Pure inductive circuit
- (c) Pure resistive circuit
- (d) None of these

10. In series LCR circuit, the phase angle between supply voltage and current is

- (a)  $\tan \phi = \frac{X_L - X_C}{R}$
- (b)  $\tan \phi = \frac{R}{X_L - X_C}$
- (c)  $\tan \phi = \frac{R}{X_L + X_C}$
- (d)  $\tan \phi = \frac{X_L + X_C}{R}$

**Very Short:**

1. The instantaneous current flowing from an ac source is  $I = 5 \sin 314 t$ . What is the rms value of current?
2. The instantaneous emf of an ac source is given by  $E = 300 \sin 314 t$ . What is the rms value of emf?
3. Give the phase difference between the applied ac voltage and the current in an LCR circuit at resonance.
4. What is the phase difference between the voltage across the inductor and the capacitor in an LCR circuit?
5. What is the power factor of an LCR series circuit at resonance?
6. In India, the domestic power supply is at 220 V, 50 Hz, while in the USA it is 110 V, 50 Hz. Give one advantage and one disadvantage of 220 V supply over 110 V supply.
7. Define the term 'wattless current'. (CBSE Delhi 2011)
8. In a series LCR circuit,  $V_L = V_C \neq V_R$ . What is the value of the power factor? (CBSE AI 2015)
9. Define capacitor reactance. Write its SI units. (CBSE Delhi 2015)
10. Define quality factor in series LCR circuit. What is its SI unit? (CBSE Delhi 2016)

### Short Questions:

1. State the phase relationship between the current flowing and the voltage applied in an ac circuit for (i) a pure resistor (ii) a pure inductor.
2. A light bulb is in turn connected in a series (a) across an LR circuit, (b) across an RC circuit, with an ac source. Explain, giving the necessary mathematical formula, the effect on the brightness of the bulb in case (a) and (b), when the frequency of the ac source is increased. (CBSE 2019C)
3. An air-core solenoid is connected to an ac source and a bulb. If an iron core is inserted in the solenoid, how does the brightness of the bulb change? Give reasons for your answer.
4. A bulb and a capacitor are connected in series to an ac source of variable frequency. How will the brightness of the bulb change on increasing the frequency of the ac source? Give reason.
5. An ideal inductor is in turn put across 220 V, 50 Hz, and 220 V, 100 Hz supplies. Will the current flowing through it in the two cases be the same or different?
6. State the condition under which the phenomenon of resonance occurs in a series LCR circuit, plot a graph showing the variation of current with a frequency of ac source in a series LCR circuit.
7. Give two advantages and two disadvantages of ac over dc.
8. In a series, LCR circuit connected to an ac source of variable frequency and voltage  $v = v_m \sin \omega t$ , draw a plot showing the variation of current ( $I$ ) with angular frequency ( $\omega$ ) for two

different values of resistance  $R_1$  and  $R_2$  ( $R_1 > R_2$ ). Write the condition under which the phenomenon of resonance occurs. For which value of the resistance out of the two curves, a sharper resonance is produced? Define the Q-factor of the circuit and give its significance. (CBSE Delhi 2013C)

### Long Questions:

1. Prove mathematically that the average power over a complete cycle of alternating current through an Ideal inductor is zero.
2. Draw the phasor diagram of a series LCR connected across an ac source  $V = V_0 \sin \omega t$ . Hence, derive the expression for the impedance of the circuit. Obtain the conditions for the phase angle under which the current is
  - (i) maximum and
  - (ii) minimum. (CBSE AI 2019)

### Assertion and Reason Question:

1. For two statements are given-one labelled Assertion (A) and the other labelled Reason (R). Select the correct answer to these questions from the codes (a), (b), (c) and (d) as given below.

- a) Both A and R are true and R is the correct explanation of A.
- b) Both A and R are true but R is not the correct explanation of A.
- c) A is true but R is false.
- d) A is false and R is also false.

**Assertion:** A bulb connected in series with a solenoid is connected to A.C. source. If a soft iron core is introduced in the solenoid, the bulb will glow brighter.

**Reason:** On introducing soft iron core in the solenoid, the inductance decreases.

2. For two statements are given-one labelled Assertion (A) and the other labelled Reason (R). Select the correct answer to these questions from the codes (a), (b), (c) and (d) as given below.

- a) Both A and R are true and R is the correct explanation of A.
- b) Both A and R are true but R is not the correct explanation of A.
- c) A is true but R is false.
- d) A is false and R is also false.


**Assertion:** An alternating current shows magnetic effect.

**Reason:** Magnitude of alternating current varies with time.

### Case Study Questions:

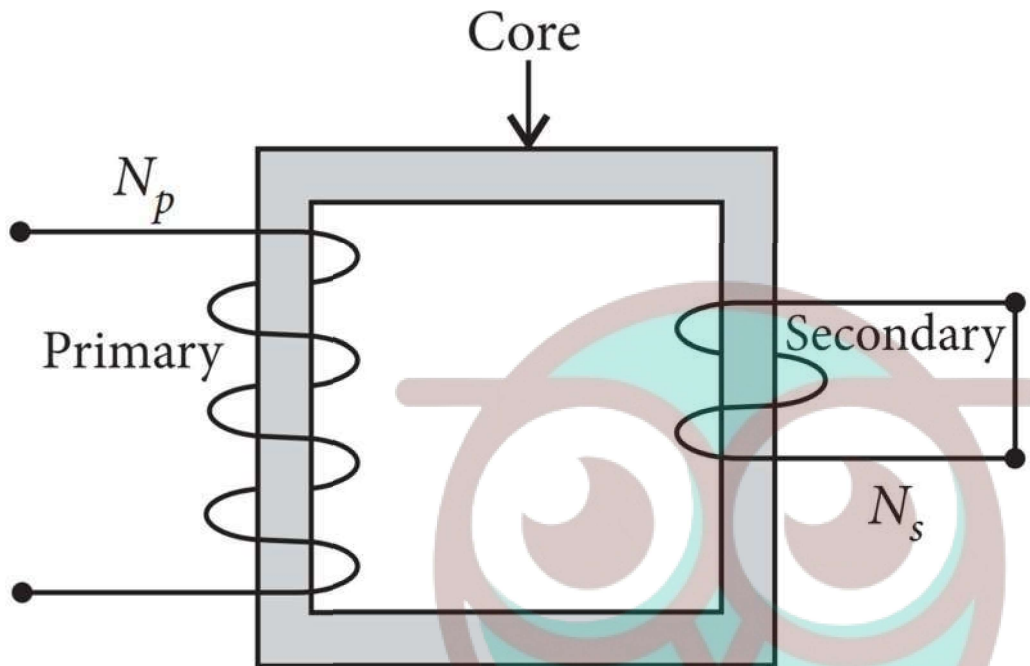1. Step-down transformers are used to decrease or step-down voltages. These are used when voltages need to be lowered for use in homes and factories. A small town with a demand of

800kW of electric power at 220V is situated 15km away from an electric plant generating power at 440V. The resistance of the two wire line carrying power is  $0.5\Omega$  per km. The town gets power from the line through a 4000 - 220V step-down transformer at a sub-station in the town.



- (i) The value of total resistance of the wires is:
- $25\Omega$
  - $30\Omega$
  - $35\Omega$
  - $15\Omega$
- (ii) The line power loss in the form of heat is:
- 550kW
  - 650kW
  - 600kW
  - 700kW
- (iii) How much power must the plant supply, assuming there is negligible power loss due to leakage?
- 600kW
  - 1600kW
  - 500W
  - 1400kW
- (iv) The voltage drop in the power line is:
- 1700V
  - 3000V


- c) 2000V
- d) 2800V

(v) The total value of voltage transmitted from the plant is:

- a) 500V
- b) 4000V
- c) 3000V
- d) 7000V

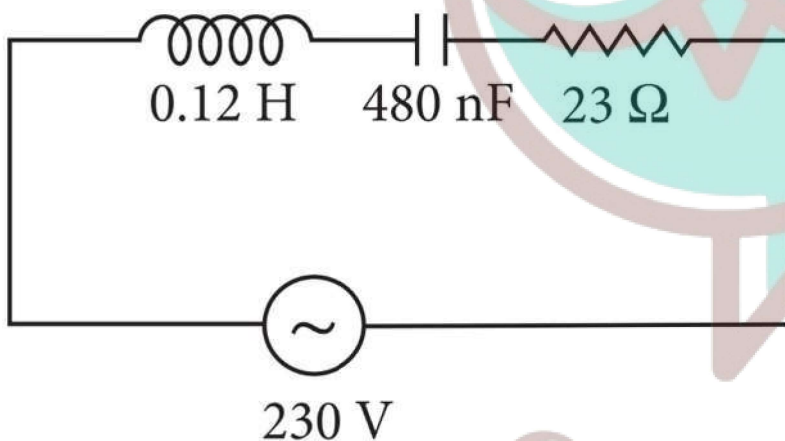2. When the frequency of ac supply is such that the inductive reactance and capacitive reactance become equal, the impedance of the series LCR circuit is equal to the ohmic resistance in the circuit. Such a series LCR circuit is known as resonant series LCR circuit and the frequency of the ac supply is known as resonant frequency. Resonance phenomenon is exhibited by a circuit only if both L and C are present in the circuit. We cannot have resonance in a RL or RC circuit.

A series LCR circuit with  $L = 0.12\text{H}$ ,  $C = 480\text{nF}$ ,  $R = 23\Omega$  is connected to a 230V variable frequency supply.



(i) Find the value of source frequency for which current amplitude is maximum.

- a) 222.32Hz
- b) 550.52Hz
- c) 663.48Hz
- d) 770Hz

(ii) The value of maximum current is:

- a) 14.14A
- b) 22.52A
- c) 50.25A
- d) 47.41A

(iii) The value of maximum power is:

- a) 2200W
- b) 2299.3W



- c) 5500W
- d) 4700W

(iv) What is the Q-factor of the given circuit?

- a) 25
- b) 42.21
- c) 35.42
- d) 21.74

(v) At resonance which of the following physical quantity is maximum?

- a) Impedance
- b) Current
- c) Both (a) and (b)
- d) Neither (a) nor (b)

A stylized owl logo with large eyes and a beak, rendered in a light teal and brown color scheme. The owl is positioned behind the 'Answer Key' text.

✓ Answer Key:

### Multiple Choice Answers-

1. Answer: b
2. Answer: c
3. Answer: b
4. Answer: b
5. Answer: b
6. Answer: c
7. Answer: c
8. Answer: c
9. Answer: c
10. Answer: a

### Very Short Answers:

1. Answer:

The rms value of current is  $\frac{5}{\sqrt{2}}$ .

2. Answer:

The rms value of voltage is  $\frac{300}{\sqrt{2}}$

3. Answer:

The applied ac voltage and the current in an LCR circuit at resonance are in phase.

Hence phase difference = 0.

4. Answer: The phase difference is  $180^\circ$ .
5. Answer: The power factor is one.
6. Answer:  
Advantage: less power loses  
Disadvantage: more fatal.
7. Answer: It is the current at which no power is consumed.
8. Answer: One.
9. Answer: It is the opposition offered to the flow of current by a capacitor. It is measured in ohm.
10. Answer: The quality factor is defined as the ratio of the voltage developed across the capacitor or inductor to the applied voltage. It does not have any unit.

### Short Questions Answers:

1. Answer:

(i) Electric current and voltage applied in a pure resistor are in same phase, i.e.  $\Phi = 0^\circ$

(ii) Applied voltage leads electric current flowing through pure-inductor in an ac circuit by phase angle of  $\pi/2$ .

2. Answer:

a) The current in LR circuit is given by

$$I = \frac{V}{\sqrt{R^2 + \omega^2 L^2}}$$

When the frequency of ac source  $\omega$  increases,  $I$  decreases, and hence brightness decreases.

(b) The current in RC circuit is given by

$$I = \frac{V}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

When the frequency of ac source  $\omega$  increases,  $I$  increases, and hence brightness increases.

3. Answer: Insertion of an iron core in the solenoid increases its inductance. This in turn increases the value of inductive reactance. This decreases the current and hence the brightness of the bulb.

4. Answer:

When the frequency of the ac is increased, it will decrease the impedance of the circuit as  $Z = \sqrt{R^2 + (1/2\pi fC)^2}$ . As a result, the current and hence the brightness of the bulb will increase.

5. Answer:


The current through the inductor is given by  $I = \frac{V}{X_L} = \frac{V}{2\pi fL}$ . The current is inversely proportional to the frequency of applied ac.

6. Answer: The phenomenon occurs when the inductive reactance becomes equal to the capacitive reactance., i.e.,  $X_L = X_C$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

The graph is as shown below.

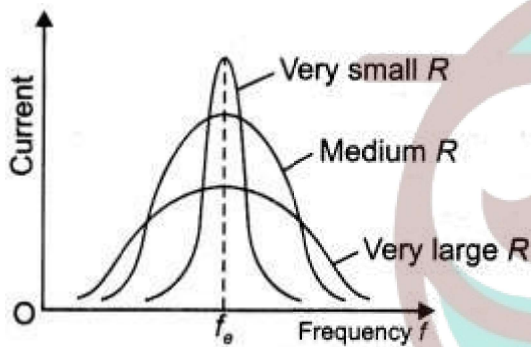

7. Answer:

Advantages of ac:


- (a) The generation and transmission of ac are more economical than dc.
- (b) The alternating voltage may be easily stepped up or down as per need by using suitable transformers.

Disadvantages of ac:

- (a) It is more fatal than dc.
- (b) It cannot be used for electrolysis.

8. Answer:

The plot is as shown.

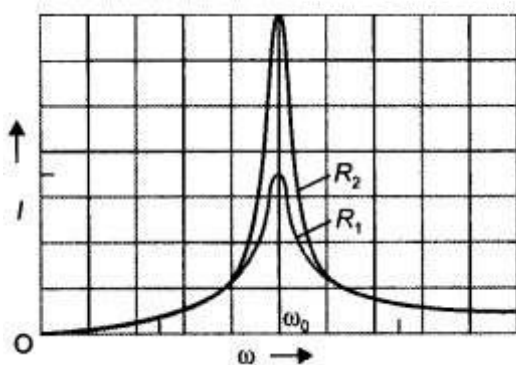

Resonance occurs in an LCR circuit when

$$X_L = X_C.$$

The smaller the value of R sharper is the resonance. Therefore, the curve will be sharper for  $R_2$ . It determines the sharpness of the resonance. The larger the value of Q sharper is the resonance.

## Long Questions Answers:

1. Answer:

Let the instantaneous value of voltage and current in the ac circuit containing a pure inductor are

$$V = V_m \sin \omega t \text{ and}$$

$$I = I_m \sin (\omega t - \pi/2) = -I_m \cos \omega t$$

where  $\pi/2$  is the phase angle by which voltage Leads current when ac flows through an inductor. Suppose the voltage and current remain constant for a small-time  $dt$ . Therefore, the electrical energy consumed in the small-time  $dt$  is

$$dW = V I dt$$

The total electrical energy consumed in one time period of ac is given by

$$W = \int_0^T VI dt = -\int_0^T V_m \sin \omega t \cdot I_m \cos \omega t dt$$

$$= -V_m I_m \int_0^T \sin \omega t \cos \omega t dt$$

$$\text{or } W = -\frac{I_m V_m}{2} \int_0^T 2 \sin \omega t \cos \omega t dt$$

$$\text{or } W = -\frac{I_m V_m}{2} \int_0^T \sin 2\omega t dt$$

$$\text{or } W = -\frac{I_m V_m}{2} \left[ -\frac{\cos(2\omega t)}{2\omega} \right]_0^T = 0$$

Therefore, the total electrical energy consumed in an ac circuit by a pure inductor is  $W = 0$

Now average power is defined as the ratio of the total electrical energy consumed over the entire cycle to the time period of the cycle, therefore


$$P_{av} = \frac{W}{T} = 0$$

Hence, the average power consumed in an ac circuit by a pure inductor is  $P_{av} = 0$

Thus, a pure inductor does not consume any power when ac flows through it. Whatever energy is used in building up current is returned during the decay of current.

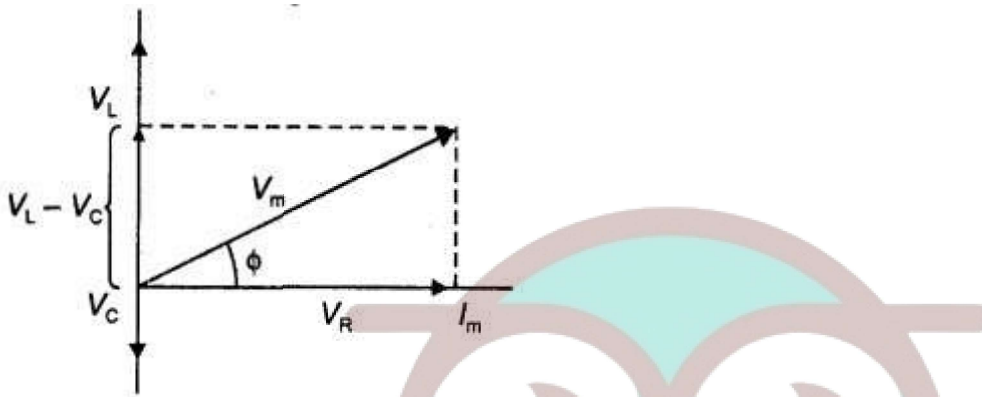2. Answer:

The voltages across the various elements are drawn as shown in the figure below.



From the diagram, we observe that the vector sum of the voltage amplitudes  $V_R$ ,  $V_L$ , and  $V_C$  equals a phasor whose length is the maximum applied voltage  $V_m$ , where the phasor  $V_m$  makes an angle  $\phi$  with the current phasor  $I_m$ . Since the voltage phasors,  $V_L$  and  $V_C$  are in opposite direction, therefore, a difference phasor  $(V_L - V_C)$  is drawn which is perpendicular to the phasor  $V_R$ . Adding vectorially we have

$$V_m = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= \sqrt{(I_m R)^2 + (I_m X_L - I_m X_C)^2}$$

$$\text{or } V_m = I_m \sqrt{R^2 + (X_L - X_C)^2}$$

where  $X_L = \omega L$  and  $X_C = 1 / \omega C$ , therefore, we can express the maximum current as

$$I_m = \frac{V_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

The impedance  $Z$  of the circuit is defined as  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

For maximum  $I_m$ ,  $Z$  should be minimum ( $Z = R$ ) or  $X_C = X_L = 0$  and  $\Phi = 0$

For  $(I_m)_{\min}$   $\Phi \rightarrow 90^\circ$  ( $|X_C - X_L| \gg R$ )  $Z \rightarrow \infty$

### Assertion and Reason Answers:

1. (d) A is false and R is also false.

#### Explanation:

On introducing soft iron core, the bulb will glow dimmer. This is because on introducing soft iron core in the solenoid, its inductance  $L$  increases, the inductive reactance,  $X_L = \omega L$  increases and hence the current through the bulb decreases.

2. (b) Both A and R are true but R is not the correct explanation of A.

**Explanation:**

Like direct current, an alternating current also produces magnetic field. But the magnitude and direction of the field goes on changing continuously with time.

**Case Study Answers:**

**1. Answer :**

(i) (d)  $15\Omega$

**Explanation:**

Resistance of the two wire lines carrying power =  $0.5 \frac{\Omega}{\text{Km}}$

Total resistance =  $(15 + 15)0.5 = 15\Omega$

(ii) (c) 600kW

**Explanation:**

Line power loss =  $I^2R$

RMS current in the coil,

$$I = \frac{P}{V_1} = \frac{800 \times 10^3}{4000} = 200A$$

$\therefore$  Power loss =  $(200)^2 \times 15 = 600kW$

(iii) (d) 1400kW

**Explanation:**

Assuming that the power loss is negligible due to the leakage of the current.

The total power supplied by the plant,

=  $800kW + 600kW = 1400kW$

(iv) (b) 3000V

**Explanation:**

Voltage drop in the power line =  $IR$

=  $200 \times 15 = 3000V$

(v) (d) 7000V

**Explanation:**

Total voltage transmitted from the plant,

=  $3000V + 4000V = 7000V$

## 2. Answer :

i. (c) 663.48Hz

**Explanation:**Here,  $L = 0.12\text{H}$ ,  $e = 480\text{nF} = 480 \times 10^{-9}\text{F}$ 

$$R = 23\Omega, V = 230\text{V}$$

$$V_0 = \sqrt{2} \times 230 = 325.22\text{V}$$

$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\text{At resonance, } \omega L - \frac{1}{\omega C} = 0$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.12 \times 480 \times 10^{-9}}} = 4166.67 \text{ rad s}^{-1}$$

$$v_R = \frac{4166.67}{2 \times 3.14} = 663.48\text{Hz}$$

ii. (a) 14.14A

**Explanation:**

$$\text{Current, } I_0 = \frac{V_0}{R} = \frac{325.22}{23} = 14.14\text{A}$$

iii. (b) 2299.3W

**Explanation:**

$$\begin{aligned} \text{Maximum power, } P_{\max} &= \frac{1}{2} (I_0)^2 R \\ &= \frac{1}{2} \times (14.14)^2 \times 23 = 2299.3\text{W} \end{aligned}$$

iv. (d) 21.74

**Explanation:**

$$\begin{aligned} \text{Quality factor, } Q &= \frac{X_R}{R} = \frac{\omega_r L}{R} \\ &= \frac{4166.67 \times 0.12}{23} = 21.74 \end{aligned}$$

v. (b) Current